

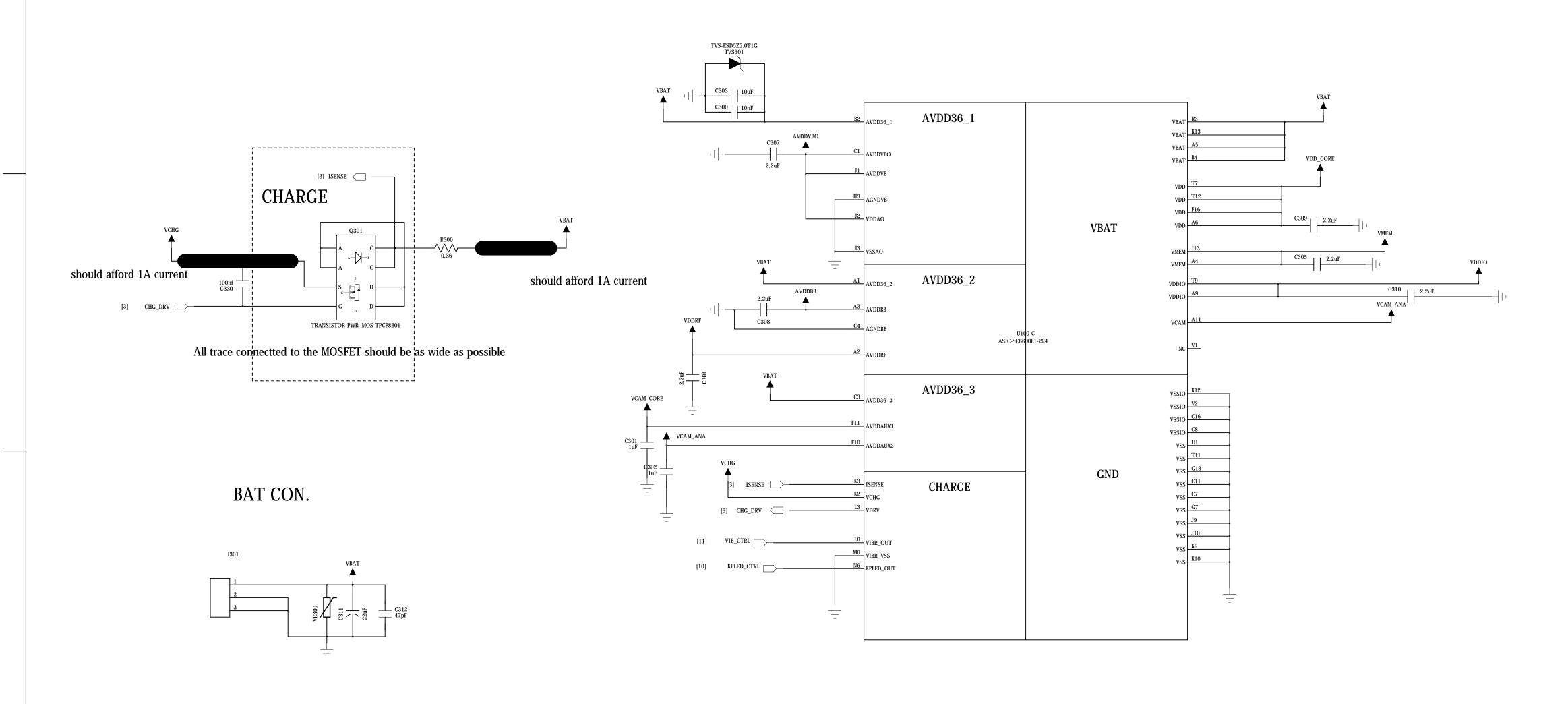


Freecom		
Project£ ^o	<pre><pre><pre><pre></pre></pre></pre></pre>	Design by£° < Design>
Title£o	<title></td><td>Check by£° <check></td></tr><tr><td>REV£o</td><td><REV></td><td>Approve£° <appr></td></tr><tr><td>File NO.£°</td><td><file no></td><td>sheet: 2 / 13</td></tr></tbody></table></title>	

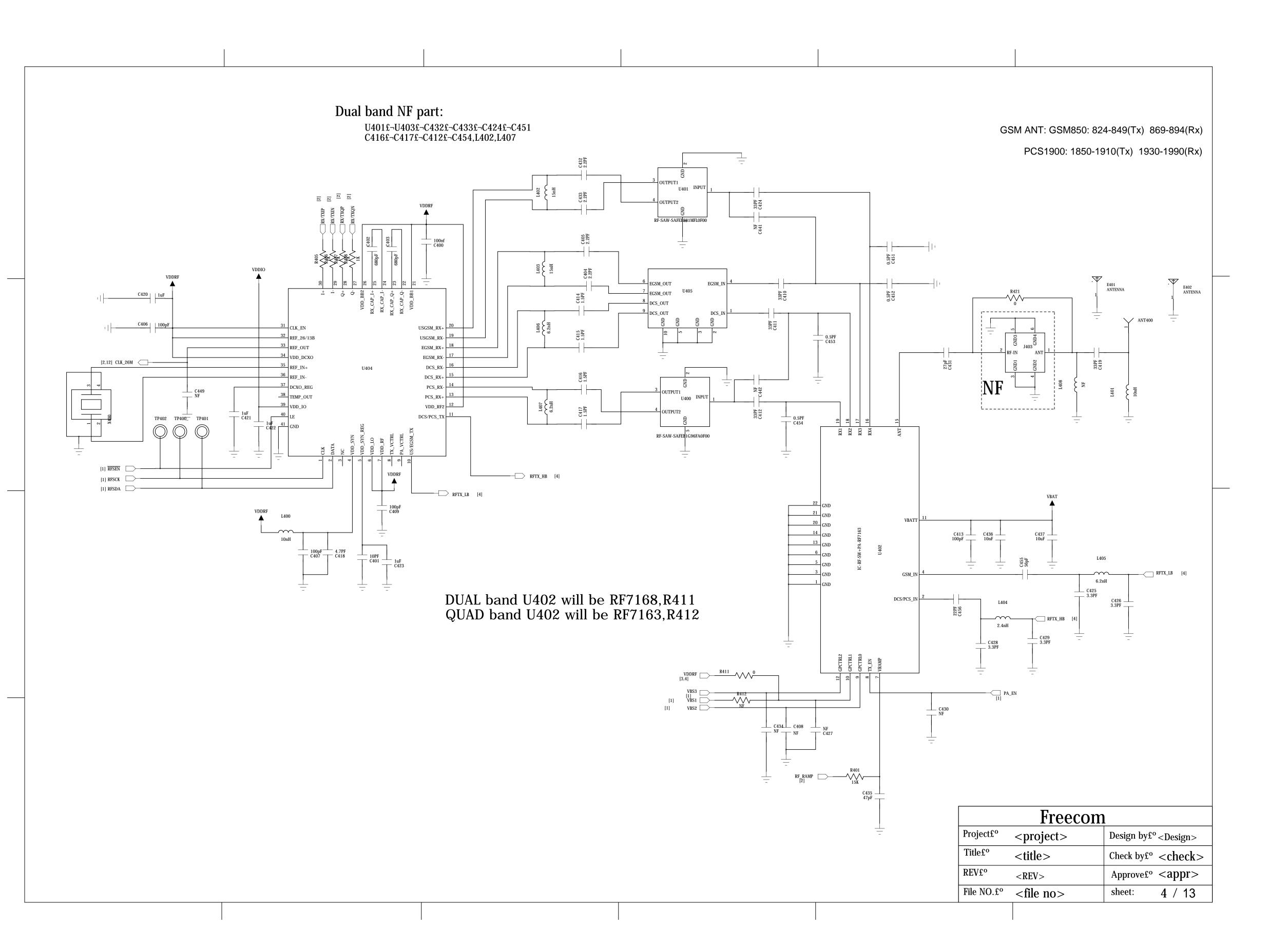


Freecom		
Project£°	<pre><pre><pre><pre></pre></pre></pre></pre>	Design by£° < Design>
Title£o	<title></td><td>Check by£° <check></td></tr><tr><td>REV£º</td><td><REV></td><td>Approve£° <appr></td></tr><tr><td>File NO.£°</td><td><file no></td><td>sheet: 3 / 13</td></tr></tbody></table></title>	

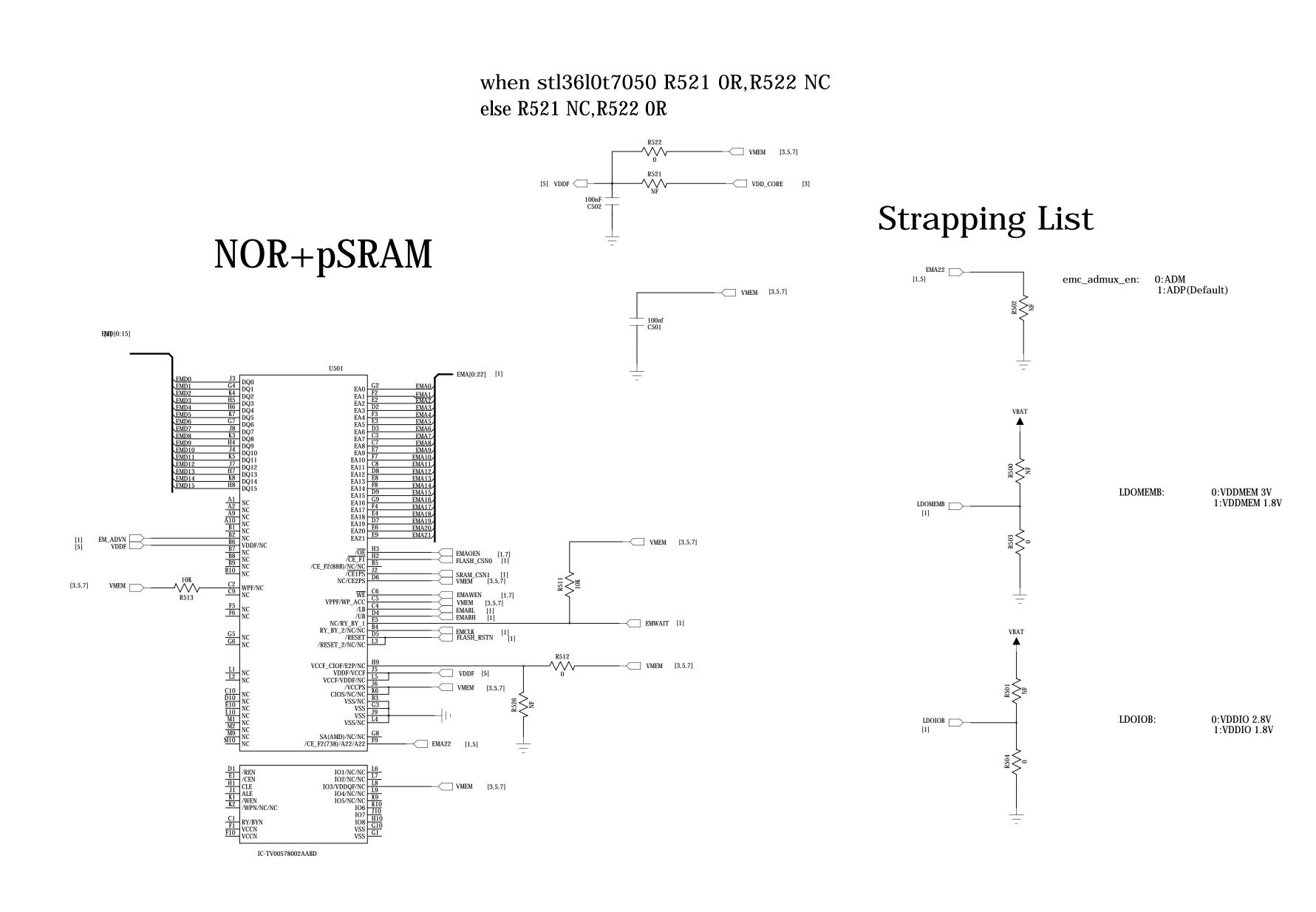




CAUTION: MCP signals have higher speed than before, layout carefully

Freecom		
>		
•		
>		

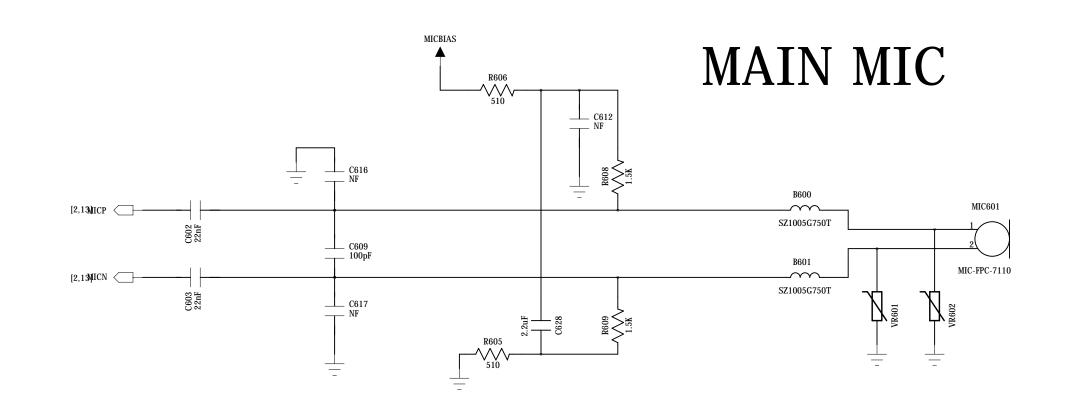


RECEIVER

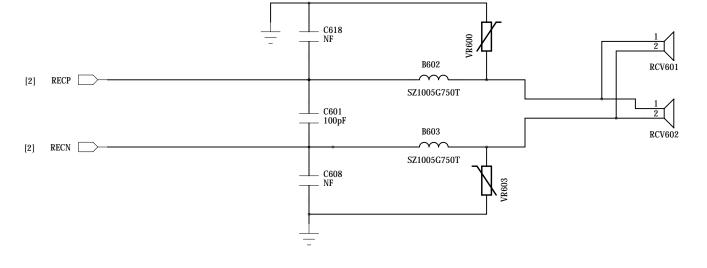


If use combined speaker and receiver ,then Analog switch are needed to prevent reverse current.Pls refer to <<SC6600H Speaker&Receiver Application Notes>>


Class AB

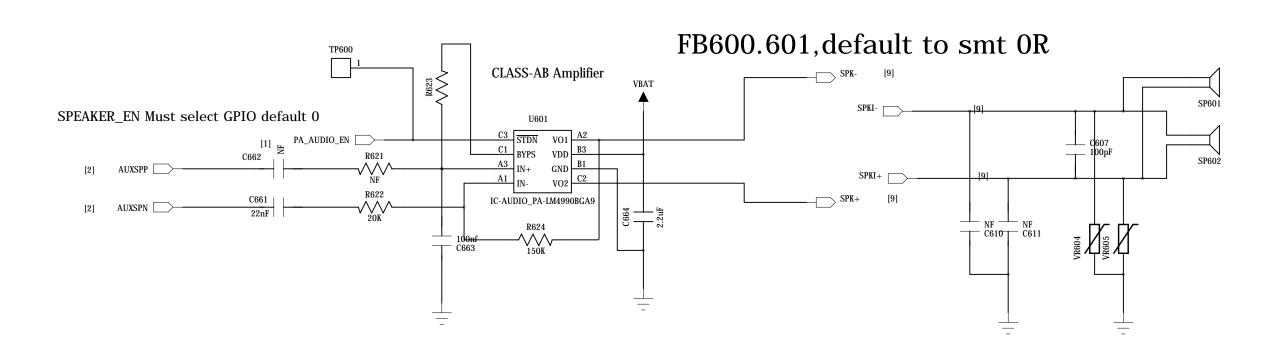


EAR-MIC

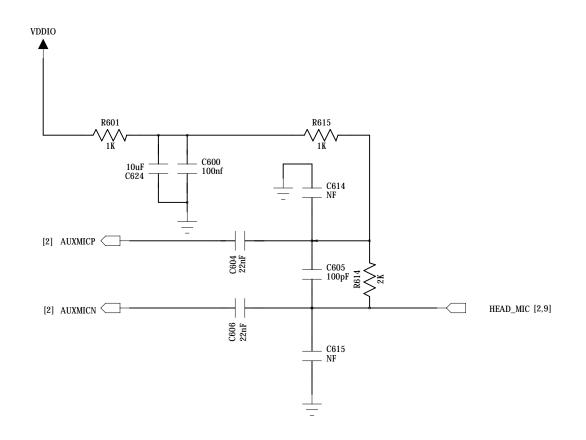


HEADPHONE

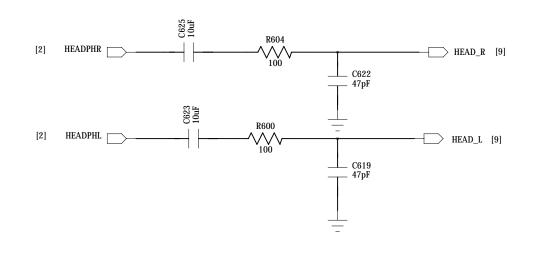


Freecom		
Project£°	<pre><pre><pre><pre></pre></pre></pre></pre>	Design by£° <design></design>
Title£o	<title></td><td>Check by£° <check></td></tr><tr><td>REV£º</td><td><REV></td><td>Approve£° <appr></td></tr><tr><td>File NO.£°</td><td><file no></td><td>sheet: 6 / 13</td></tr></tbody></table></title>	

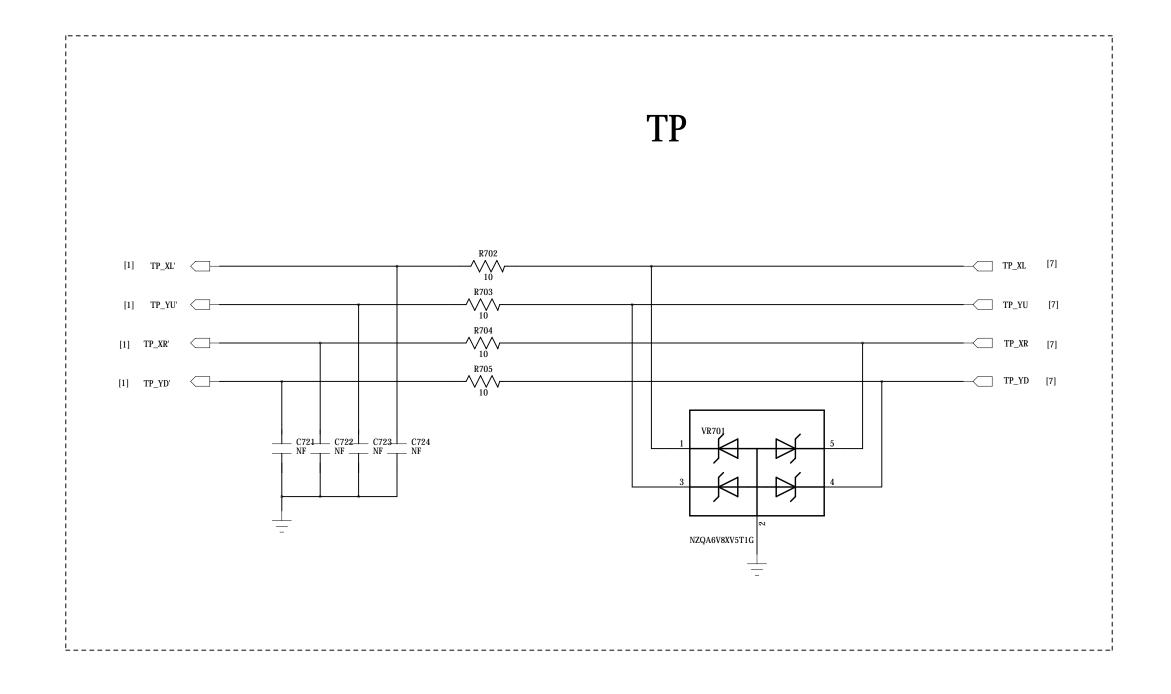


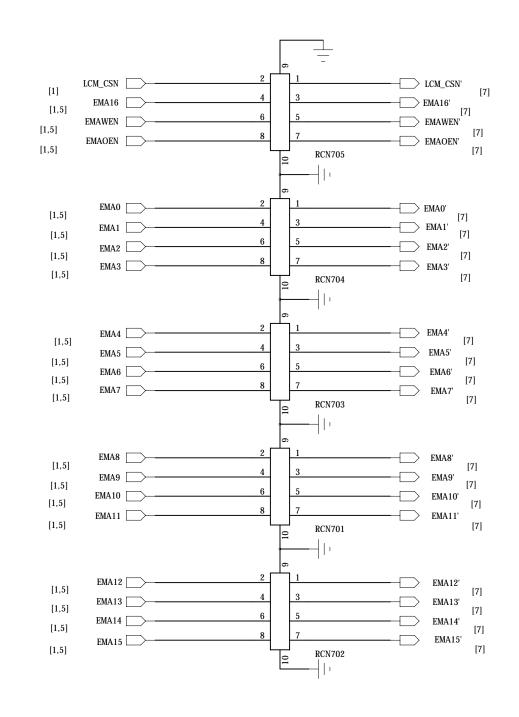


LCM_2.2-QVGA"//QCIF"

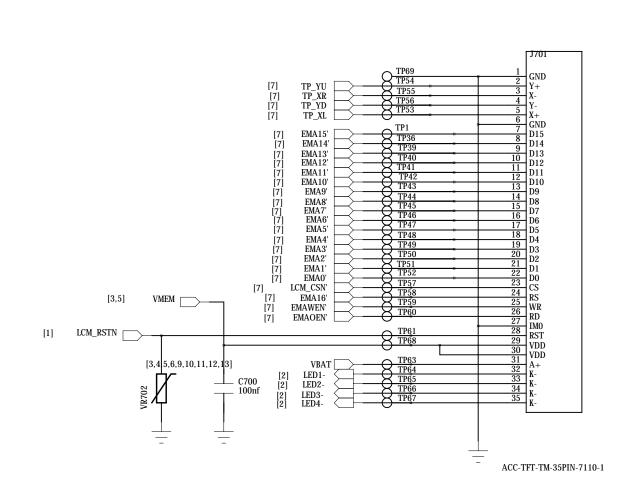


Freecom		
Project£ ^o	<pre><pre><pre><pre></pre></pre></pre></pre>	Design by£° < Design>
Title£°	<title></td><td>Check by£° <check></td></tr><tr><td>REV£º</td><td><REV></td><td>Approve£o <appr></td></tr><tr><td>File NO.£°</td><td><file no></td><td>sheet: 7 / 13</td></tr></tbody></table></title>	

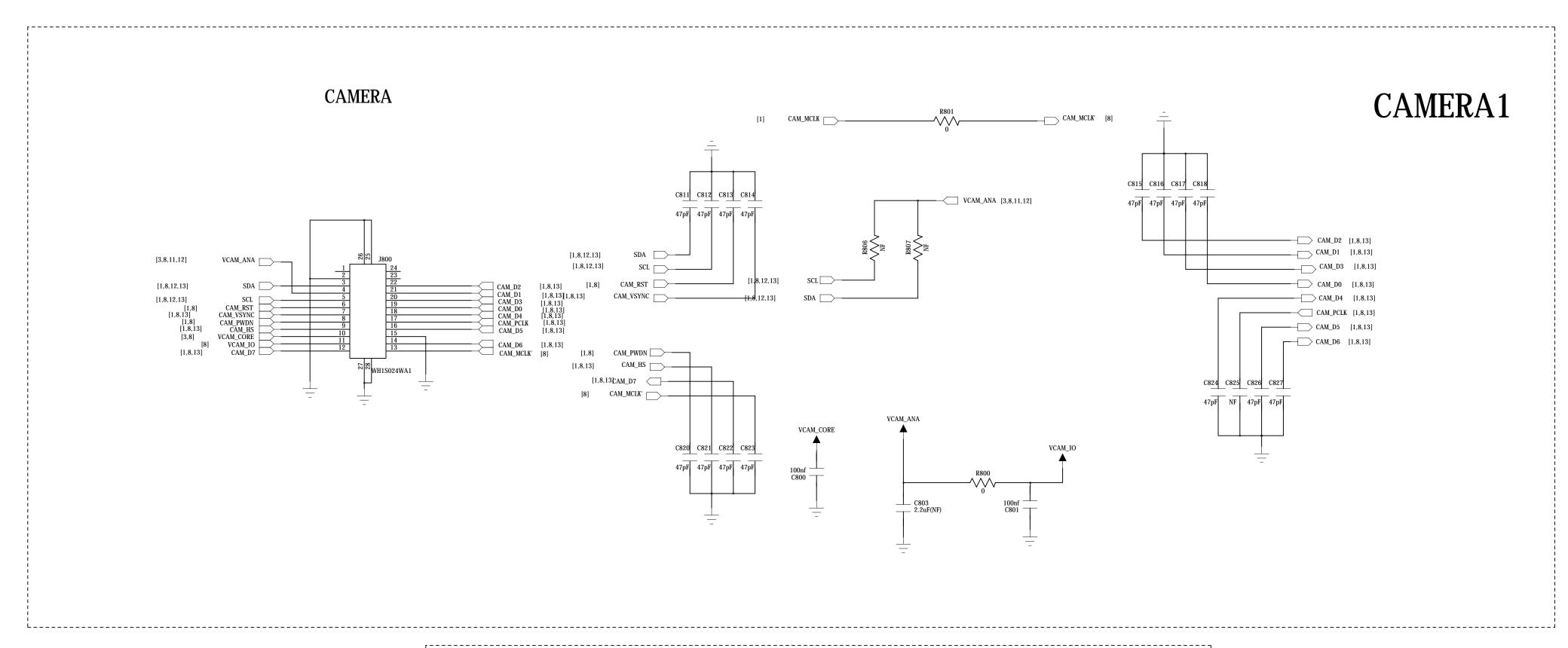


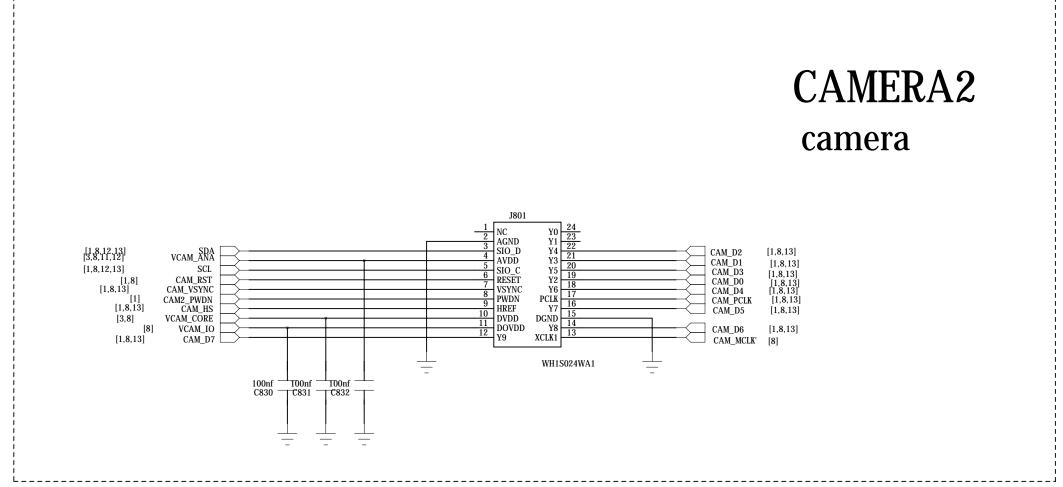



Freecom		
Project£ ^o	<pre><pre><pre><pre></pre></pre></pre></pre>	Design by£° < Design>
Title£°	<title></td><td>Check by£° <check></td></tr><tr><td>REV£o</td><td><REV></td><td>Approve£° <appr></td></tr><tr><td>File NO.£°</td><td><file no></td><td>sheet: 8 / 13</td></tr></tbody></table></title>	

INTERFACE

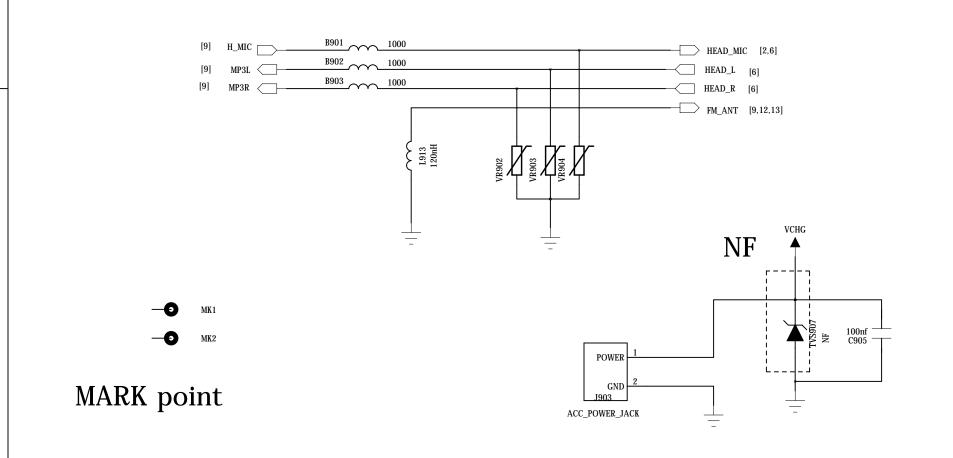

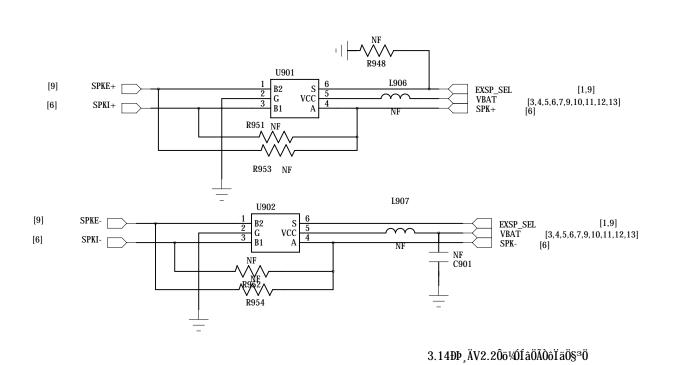

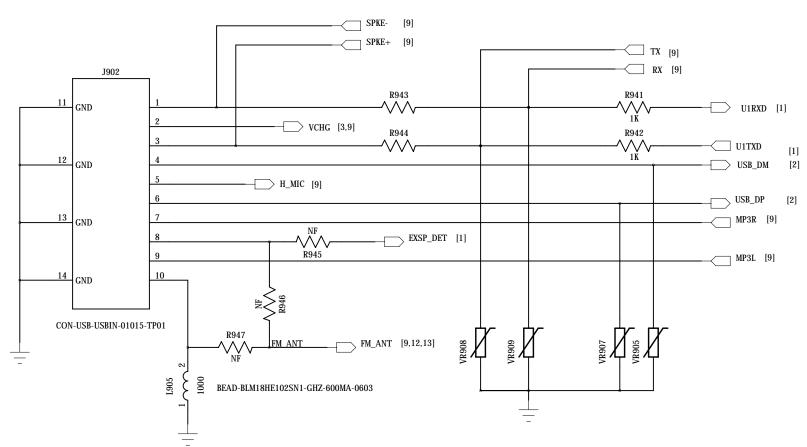

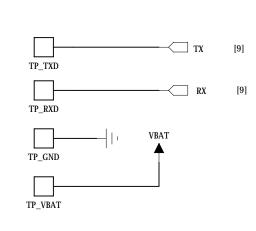


Boot select:

U0RSTN = low --> boot from USB

UORSTN = high --> boot from NOR or UART

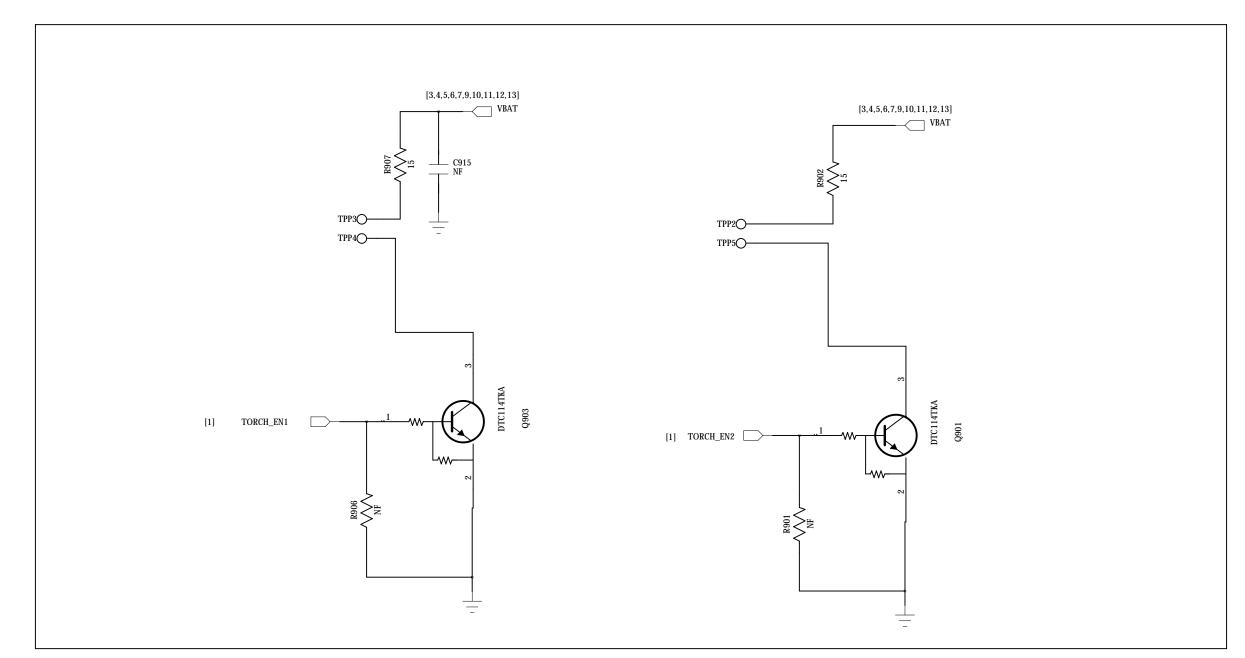
NOTE: keyin0 & keyout0 pressed when power up will also lead to USB boot




Freecom		
Project£°	<pre><pre><pre><pre></pre></pre></pre></pre>	Design by£° < Design>
Title£o	<title></td><td>Check by£° <check></td></tr><tr><td>REV£º</td><td><REV></td><td>Approve£° <appr></td></tr><tr><td>File NO.£°</td><td><file no></td><td>sheet: 9 / 13</td></tr></tbody></table></title>	

KEYPAD


KEY

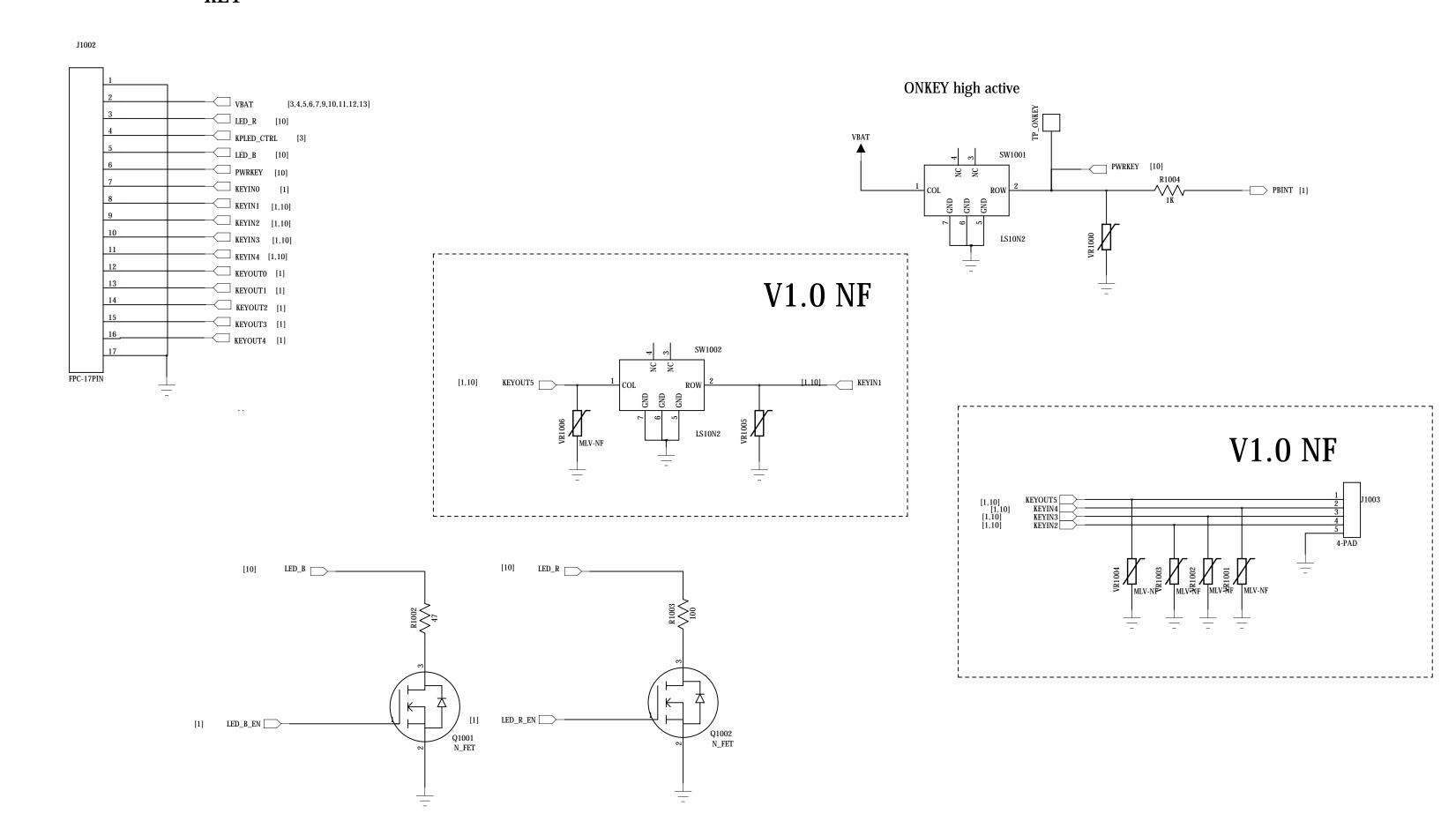



Freecom		
Project£o	<pre><pre><pre><pre></pre></pre></pre></pre>	Design by£° < Design>
Title£°	<title></th><th>Check by£° <check></th></tr><tr><th>REV£°</th><th><REV></th><th>Approve£° <appr></th></tr><tr><th>File NO.£°</th><th><file no></th><th>sheet: 10/ 13</th></tr></tbody></table></title>	

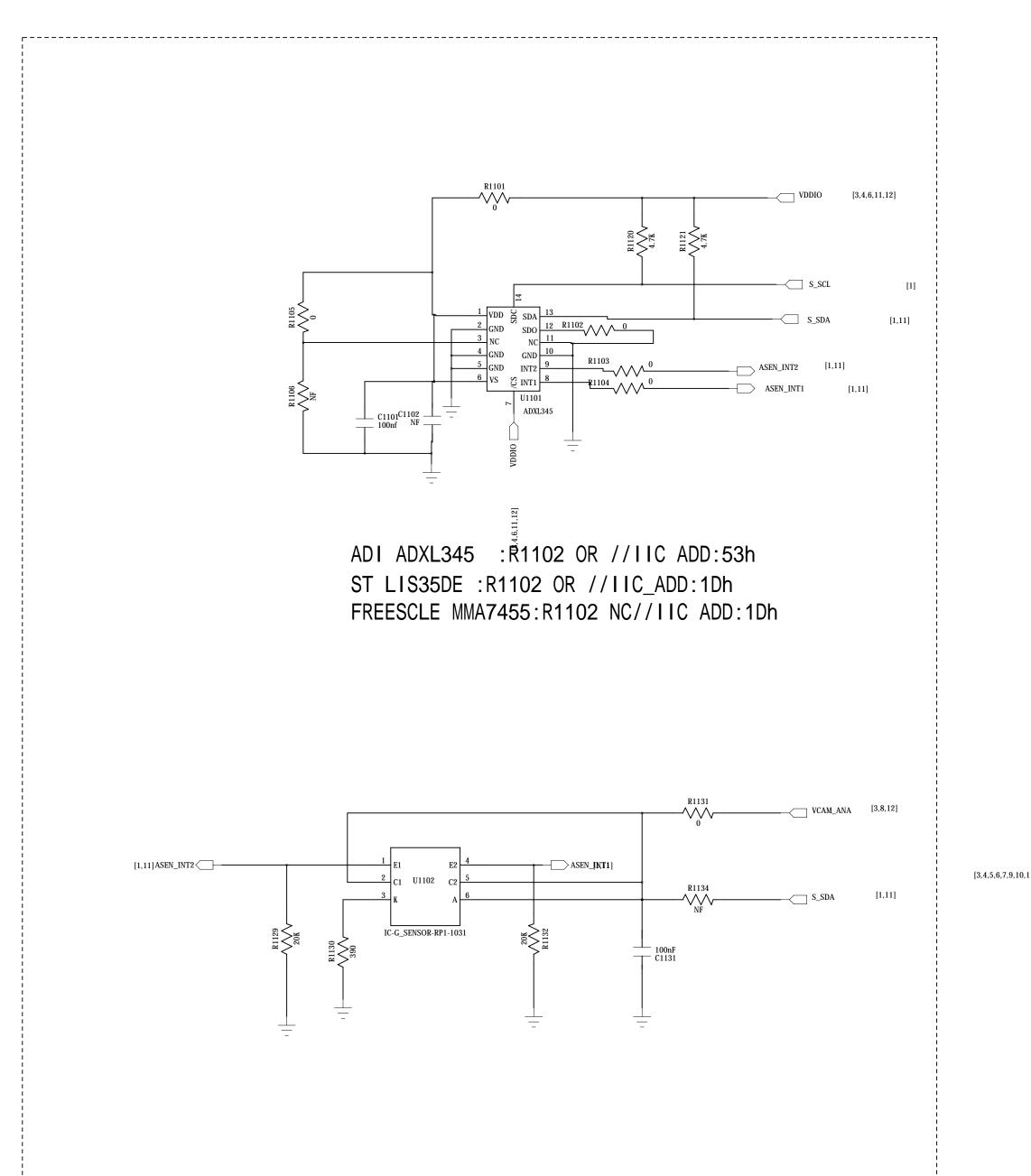


·-------

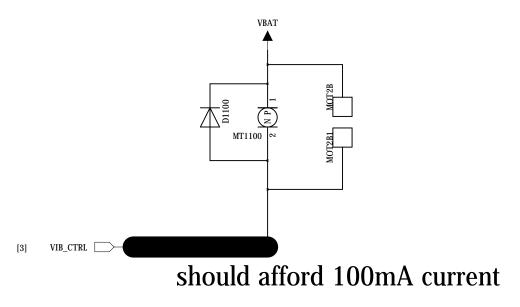


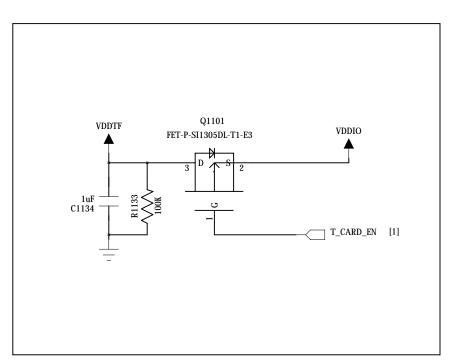

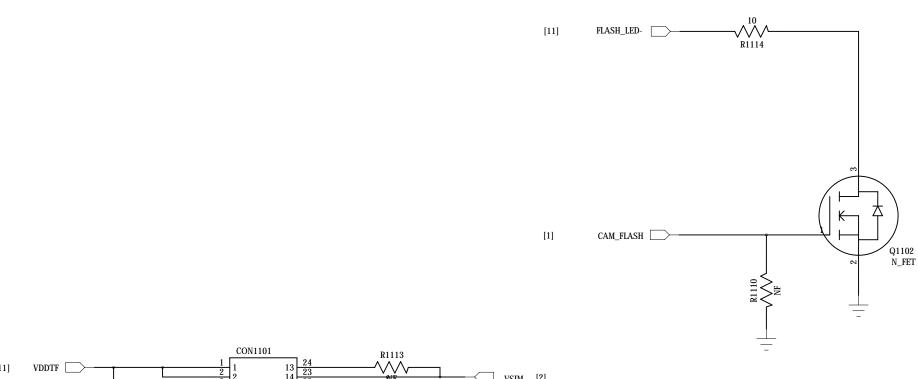

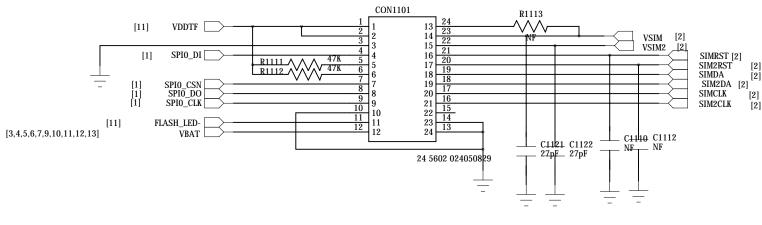

Freecom		
Project£o	<pre><pre><pre><pre></pre></pre></pre></pre>	Design by£o < Design>
Title£o	<title></td><td>Check by£° <check></td></tr><tr><td>REV£º</td><td><REV></td><td>Approve£° <appr></td></tr><tr><th>File NO.£°</th><th><file no></th><th>sheet: 11/ 13</th></tr></tbody></table></title>	

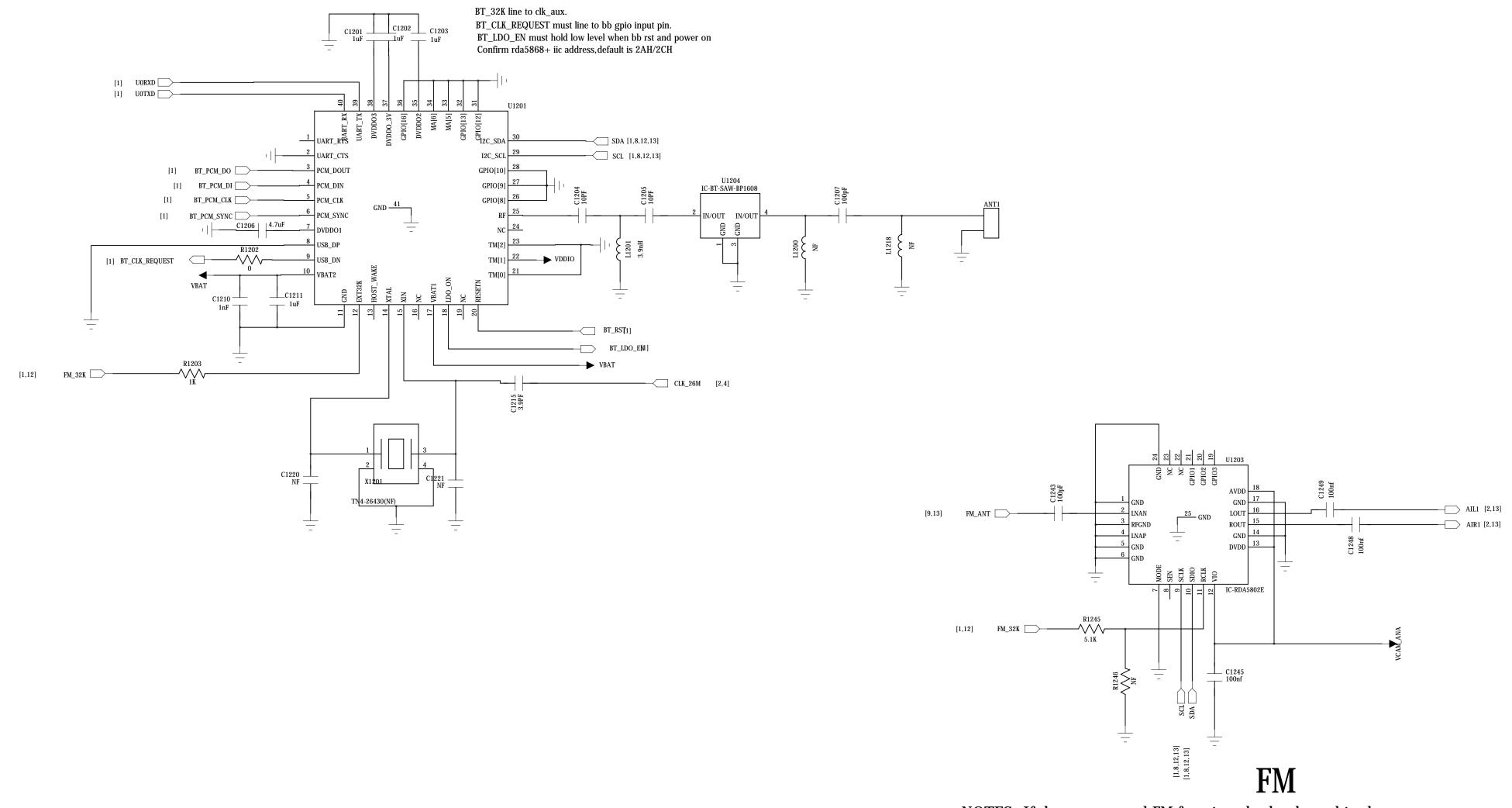

NOTES: If the camera and FM functions both adopted in the system, they should use the same IO power supply and I2C pullup resistances.

Freecom		
Project£°	<pre><pre><pre><pre></pre></pre></pre></pre>	Design by£° < Design>
Title£°	<title></td><td>Check by£° <check></td></tr><tr><td>REV£°</td><td><REV></td><td>Approve£o <appr></td></tr><tr><td>File NO.£°</td><td><file no></td><td>sheet: 12/13</td></tr></tbody></table></title>	

